

Homework 1

Problem 1

A) $\{XNOR, NOR\}$ $\{AND, OR, NOT\}$

↕

$$AND = NOR\{NOR(A, A), NOR(B, B)\}$$

$$OR = NOR\{NOR(A, B)\}$$

$$NOT = NOR\{A, A\}$$

$\{XNOR, NOR\}$ is ~~not~~ a complete set as AND, OR, and NOT gate can be implemented from this set, but it's not a minimal complete set as even if we remove XNOR, it doesn't effect the completeness.

B) $\{XNOR, OR\}$

$$AND = XNOR\{OR(A, B), XNOR(A, B)\}$$

$$OR = OR(A, B)$$

$$NOT = XNOR(A, 0)$$


$\{XNOR, OR\} \rightarrow$ is a complete set and also a minimal complete set as, to construct AND gate both of the gates are required for sure.

③ {XNOR, NOT}.


↓
It is not a complete set as we cannot implement AND, OR gates using just XNOR, NOT gates.

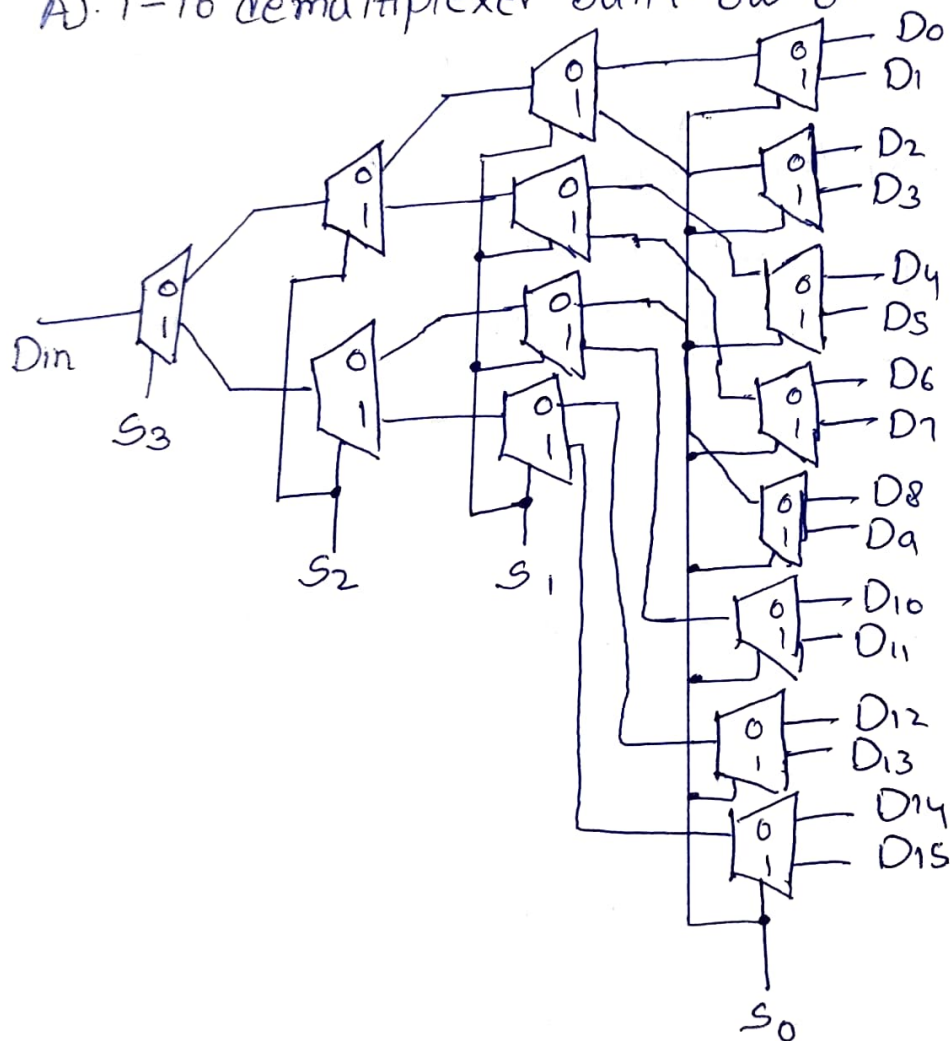Problem 3.

A). 1-16 demultiplexer built out of 1-2 demultiplexers



3) 4-16 decoder with enable built out of 2-4 decoders with enable.

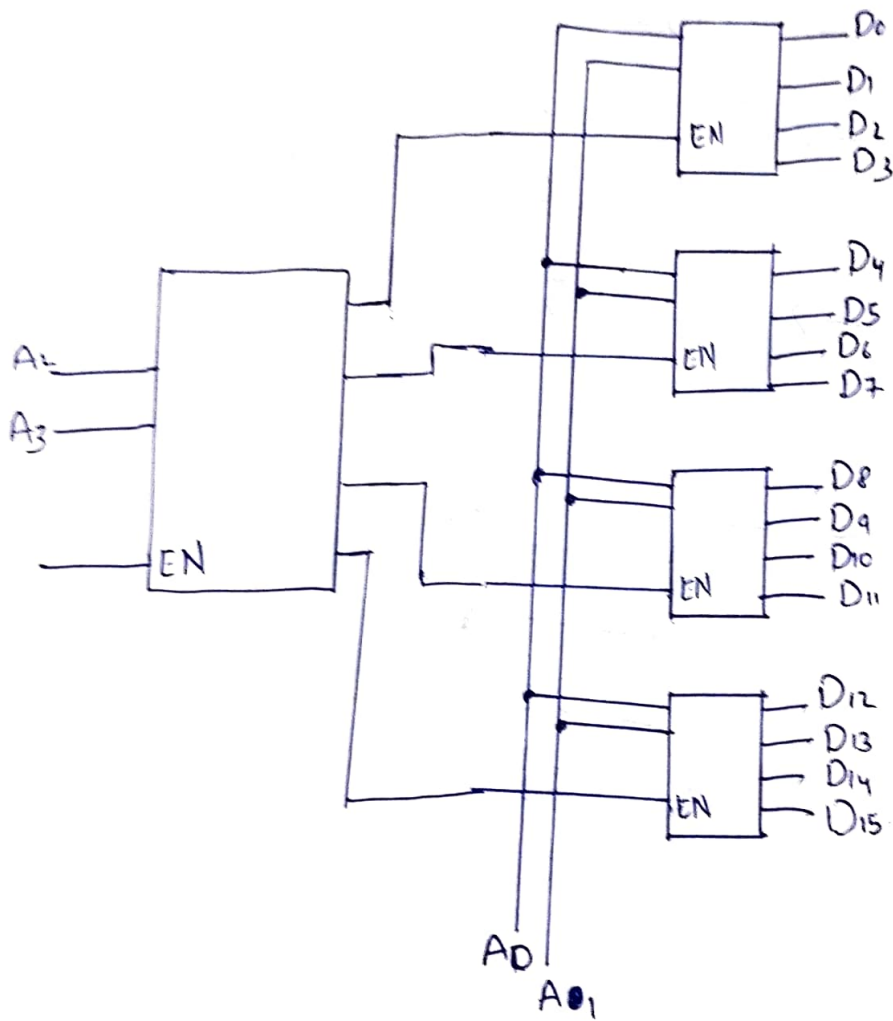

Problem 6

12 bit Address

for

	A_{11}	A_{10}	A_9	A_8	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
$01 \rightarrow$	0	0	$\rightarrow 400-47F \rightarrow e_0$									
$\rightarrow 01 \rightarrow$	0	1	$\rightarrow 480-4FF \rightarrow e_1$									
$\rightarrow 10 \rightarrow$	1	0	$\rightarrow 500-57F \rightarrow e_2$									
$\rightarrow 11 \rightarrow$	1	1	$\rightarrow 580-5FF \rightarrow e_3$									

Case B

